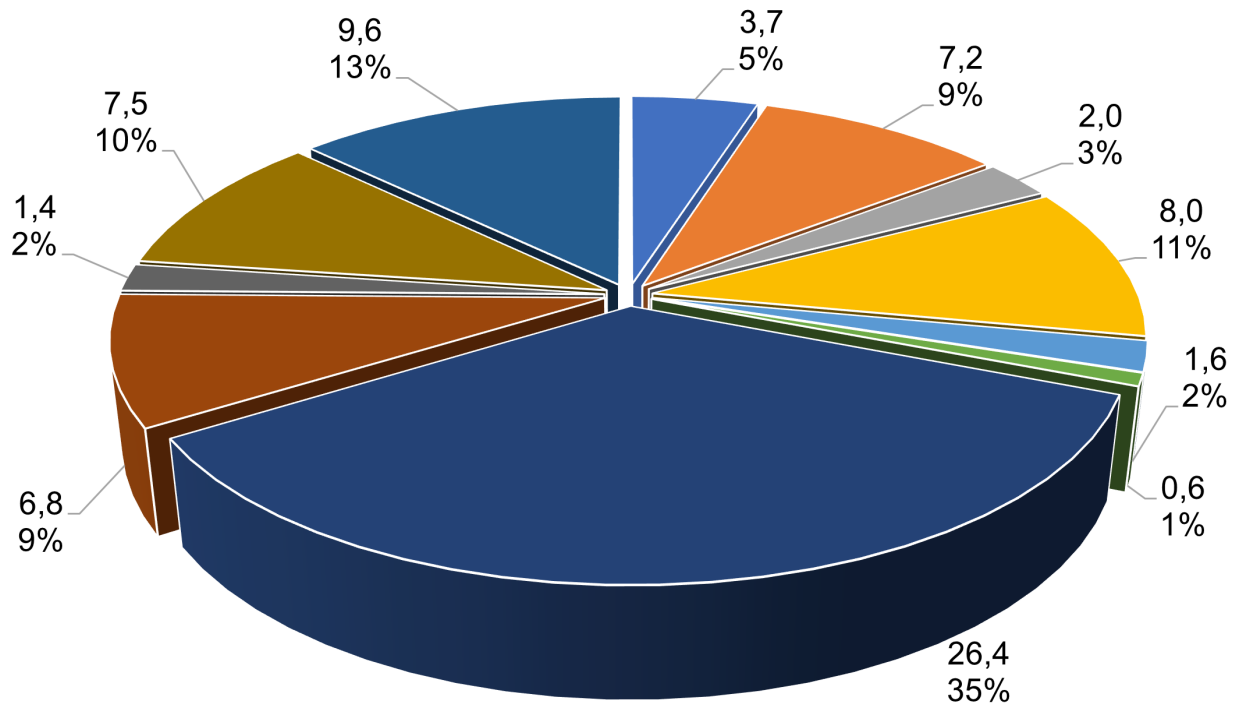


Power loss distribution estimates [W]
 $V_{in}=800V$, $V_{out}=12V$, $P_{out}=1200W$



- Input Filter
- PSFB+Gate drivers
- Shim inductor
- Transformer
- Auxiliary GD supply
- Vin sense subcircuit
- SR FETs+Gate drivers
- Output Inductors
- Output shunt resistor
- Output short-circuit switch
- Misc (PCB losses, snubbers, AUX)